

# 矩阵键盘扫描控制电路设计

徐震 PB20051102

## 实验内容

生成随时钟周期选择每一列的列选信号作为输出，键盘上的行选信号作为输入，用来实现按键数字在数码管上的显示

## 设计分析

生成随时钟周期选择每一列的列选信号作为输出，键盘上的行选信号作为输入，通过确认行和列的电平来判断是哪个按钮被按下

## 源码

```
1 module keyboard_xz(SW_R3,SW_R2,SW_R1,SW_R0,CLK,a,b,c,d,e,f,g,COM,SW_CO3,SW_CO2,SW_CO1,SW_CO0);
2 //顶层实体
3 input SW_R3,SW_R2,SW_R1,SW_R0,CLK;
4 output a,b,c,d,e,f,g,COM,SW_CO3,SW_CO2,SW_CO1,SW_CO0;
5 wire [1:0]column_chose,saved_column;
6 wire CLKD6;
7 wire [3:0]data;
8 wire [2:0]row_CHS;
9
10 DF6 U0(CLK,CLKD6);
11 counter U1(CLKD6,column_chose);
12 colum U2(column_chose,SW_CO3,SW_CO2,SW_CO1,SW_CO0);
13 row_CHS U3(SW_R3,SW_R2,SW_R1,SW_R0,row_CHS);
14 Q_save_colum U4(row_CHS,CLKD6,column_chose,saved_column);
15 judge U5(row_CHS,saved_column,data);
16 FOUR_SEVEN_DECODE U6(data,a,b,c,d,e,f,g);
17
18 assign COM=1'b1;|
19 endmodule
```

```
1 module DF6(clk,clk6d);
2 //分频器
3 input clk;
4 output clk6d;
5 reg clk6d;
6 reg [19:0] cnt;
7 always@(posedge clk)begin
8   if(cnt==20'b11111111111111111111)begin cnt<=20'b00000000000000000000;clk6d=~clk6d;end
9   else cnt<=cnt+20'b000000000000000000001;
10 end
11 endmodule
```

```
1 module counter(clk,column_chose);
2 //计数器
3 input clk;
4 output [1:0]column_chose;
5 reg [1:0]column_chose=2'b00;
6
7 always@(posedge clk)begin
8   if(column_chose==2'b11)column_chose<=2'b00;
9   else column_chose<= column_chose+2'b01;
10 end
11 endmodule
```

```

1 module colum(column_chose,SW_CO3,SW_CO2,SW_CO1,SW_CO0);
2 //生成列选信号
3 input [1:0]column_chose;
4 output SW_CO3,SW_CO2,SW_CO1,SW_CO0;
5 reg SW_CO3,SW_CO2,SW_CO1,SW_CO0;
6
7 always@(column_chose)begin
8     case(column_chose)
9         2'b00: begin SW_CO3<=1'b1;SW_CO2<=1'b1;SW_CO1<=1'b1;SW_CO0<=1'b0;end
10        2'b01: begin SW_CO3<=1'b1;SW_CO2<=1'b1;SW_CO1<=1'b0;SW_CO0<=1'b1;end
11        2'b10: begin SW_CO3<=1'b1;SW_CO2<=1'b0;SW_CO1<=1'b1;SW_CO0<=1'b1;end
12        2'b11: begin SW_CO3<=1'b0;SW_CO2<=1'b1;SW_CO1<=1'b1;SW_CO0<=1'b1;end
13    endcase
14 end
15 endmodule

```

```

1 module row CHS(SW_R3,SW_R2,SW_R1,SW_R0,row_chose);
2 //编码器，编码行选信号
3 input SW_R3,SW_R2,SW_R1,SW_R0;
4 output [2:0]row_chose;
5 reg [2:0]row_chose;
6
7 always@(SW_R3 or SW_R2 or SW_R1 or SW_R0)begin
8     case({SW_R3,SW_R2,SW_R1,SW_R0})
9         4'b1111: begin row_chose<=3'b100;end
10        4'b1110: begin row_chose<=3'b000;end
11        4'b1101: begin row_chose<=3'b001;end
12        4'b1011: begin row_chose<=3'b010;end
13        4'b0111: begin row_chose<=3'b011;end
14    endcase
15 end
16 endmodule

```

```

1 module Q save colum(row_chose,clk6d,column_chose,saved_colum);
2 //边缘触发寄存器，保留状态使输出稳定
3 input [2:0]row_chose;
4 input [1:0]column_chose;
5 input clk6d;
6 output [1:0]saved_colum;
7 reg [1:0]saved_colum;
8
9 always@(posedge clk6d)begin
10     if(row_chose!=3'b100)saved_colum<=column_chose;
11 end
12 endmodule

```

```

1  module judge(row_chose,column_chose,data);
2  //通过列选信号和行选信号判断按下的按键，输出是二进制编码的数字
3      input [2:0]row_chose;
4      input [1:0]column_chose;
5      output [3:0]data;
6      reg [3:0]data;
7
8      always@(row_chose or column_chose)
9      if(row_chose!=3'b100)begin
10         if(row_chose==3'b000)
11             case(column_chose)
12                 2'b00: begin data<=4'b0000;end
13                 2'b01: begin data<=4'b0001;end
14                 2'b10: begin data<=4'b0010;end
15                 2'b11: begin data<=4'b0011;end
16             endcase
17         else if(row_chose==3'b001)
18             case(column_chose)
19                 2'b00: begin data<=4'b0100;end
20                 2'b01: begin data<=4'b0101;end
21                 2'b10: begin data<=4'b0110;end
22                 2'b11: begin data<=4'b0111;end
23             endcase
24         else if(row_chose==3'b010)
25             case(column_chose)
26                 2'b00: begin data<=4'b1000;end
27                 2'b01: begin data<=4'b1001;end
28                 2'b10: begin data<=4'b1010;end
29                 2'b11: begin data<=4'b1011;end
30             endcase
31         else if(row_chose==3'b011)
32             case(column_chose)
33                 2'b00: begin data<=4'b1100;end
34                 2'b01: begin data<=4'b1101;end
35                 2'b10: begin data<=4'b1110;end
36                 2'b11: begin data<=4'b1111;end
37             endcase
38         end
39     endmodule

```

```

1  module FOUR_SEVEN_DECODE(data,a,b,c,d,e,f,g);
2  //47译码器，把二进制编码译制为数码管的控制信号
3      input [3:0]data;
4      output a,b,c,d,e,f,g;
5      reg [6:0]final_data;
6
7      always@(data)begin
8          case(data)
9              4'b0000: final_data<=7'b0000001;
10             4'b0001: final_data<=7'b1001111;
11             4'b0010: final_data<=7'b0010010;
12             4'b0011: final_data<=7'b0000110;
13             4'b0100: final_data<=7'b1001100;
14             4'b0101: final_data<=7'b0100100;
15             4'b0110: final_data<=7'b0100000;
16             4'b0111: final_data<=7'b0001111;
17             4'b1000: final_data<=7'b0000000;
18             4'b1001: final_data<=7'b0000100;
19             4'b1010: final_data<=7'b0001000;
20             4'b1011: final_data<=7'b1100000;
21             4'b1100: final_data<=7'b0110001;
22             4'b1101: final_data<=7'b1000010;
23             4'b1110: final_data<=7'b0110000;
24             4'b1111: final_data<=7'b0111000;
25          endcase
26      end
27      assign a=final_data[6];
28      assign b=final_data[5];
29      assign c=final_data[4];
30      assign d=final_data[3];
31      assign e=final_data[2];
32      assign f=final_data[1];
33      assign g=final_data[0];
34  endmodule


```

## 仿真


```

1 | timescale 10ns/1ns
2 | module keyboard_xz_tb();
3 |   reg SW_R3,SW_R2,SW_R1,SW_R0,CLK;
4 |   wire a,b,c,d,e,f,g,COM,SW_CO3,SW_CO2,SW_CO1,SW_CO0;
5 |
6 |   initial CLK=0;
7 |   always #1 CLK=~CLK;
8 |
9 |   initial begin
10 |     #0 SW_R3<=1'b1;#0 SW_R2<=1'b1;#0 SW_R1<=1'b1;#0 SW_R0<=1'b1;
11 |   end
12 |   always begin
13 |     #4 SW_R3<=1'b1;#0 SW_R2<=1'b1;#0 SW_R1<=1'b1;#0 SW_R0<=1'b0;
14 |     #2 SW_R3<=1'b1;#0 SW_R2<=1'b1;#0 SW_R1<=1'b0;#0 SW_R0<=1'b1;
15 |     #2 SW_R3<=1'b1;#0 SW_R2<=1'b0;#0 SW_R1<=1'b1;#0 SW_R0<=1'b1;
16 |     #2 SW_R3<=1'b0;#0 SW_R2<=1'b1;#0 SW_R1<=1'b1;#0 SW_R0<=1'b1;
17 |     #2 SW_R3<=1'b1;#0 SW_R2<=1'b1;#0 SW_R1<=1'b1;#0 SW_R0<=1'b1;
18 |   end
19 |
20 |   keyboard_xz U0(SW_R3,SW_R2,SW_R1,SW_R0,CLK,a,b,c,d,e,f,g,COM,SW_CO3,SW_CO2,SW_CO1,SW_CO0);
21 | endmodule

```

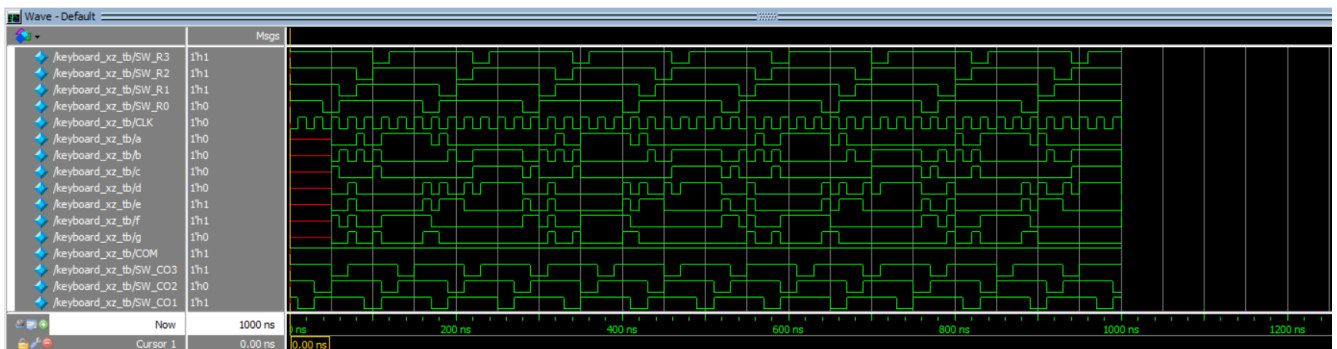

## 中间结果

 

Flow Summary	
Flow Status	Successful - Wed Nov 01 19:55:35 2023
Quartus II 64-Bit Version	13.0.1 Build 232 06/12/2013 SP 1 SJ Full Version
Revision Name	keyboard_xz
Top-level Entity Name	keyboard_xz
Family	Cyclone V
Device	5CEFA2F23C8
Timing Models	Final
Logic utilization (in ALMs)	27 / 9,430 ( < 1 % )
Total registers	27
Total pins	17 / 224 ( 8 % )
Total virtual pins	0
Total block memory bits	0 / 1,802,240 ( 0 % )
Total DSP Blocks	0 / 25 ( 0 % )
Total HSSI RX PCSs	0
Total HSSI PMA RX Deserializers	0
Total HSSI PMA RX ATT Deserializers	0
Total HSSI TX PCSs	0
Total HSSI PMA TX Serializers	0
Total HSSI PMA TX ATT Serializers	0
Total PLLs	0 / 4 ( 0 % )
Total DLLs	0 / 4 ( 0 % )

# FPGA 验证

依次按下数字键盘，均显示按下的数字，没有抖动

	Node Name	Direction	Location	I/O Bank	VREF Group	Fitter Location	I/O Standard	Reserved	Current Strengt	Slew Rate
in	CLK	Input	PIN_W16	4A	B4A_N0	PIN_W16	2.5 V (default)		12mA (default)	
out	COM	Output	PIN_C11	7A	B7A_N0	PIN_C11	2.5 V (default)		12mA (default)	1 (default)
out	SW_CO0	Output	PIN_Y17	4A	B4A_N0	PIN_Y17	2.5 V (default)		12mA (default)	1 (default)
out	SW_CO1	Output	PIN_AA20	4A	B4A_N0	PIN_AA20	2.5 V (default)		12mA (default)	1 (default)
out	SW_CO2	Output	PIN_AB20	4A	B4A_N0	PIN_AB20	2.5 V (default)		12mA (default)	1 (default)
out	SW_CO3	Output	PIN_AB22	4A	B4A_N0	PIN_AB22	2.5 V (default)		12mA (default)	1 (default)
in	SW_R0	Input	PIN_Y21	4A	B4A_N0	PIN_Y21	2.5 V (default)		12mA (default)	
in	SW_R1	Input	PIN_Y19	4A	B4A_N0	PIN_Y19	2.5 V (default)		12mA (default)	
in	SW_R2	Input	PIN_W21	4A	B4A_N0	PIN_W21	2.5 V (default)		12mA (default)	
in	SW_R3	Input	PIN_V21	4A	B4A_N0	PIN_V21	2.5 V (default)		12mA (default)	
out	a	Output	PIN_K19	7A	B7A_N0	PIN_K19	2.5 V (default)		12mA (default)	1 (default)
out	b	Output	PIN_H18	7A	B7A_N0	PIN_H18	2.5 V (default)		12mA (default)	1 (default)
out	c	Output	PIN_K20	7A	B7A_N0	PIN_K20	2.5 V (default)		12mA (default)	1 (default)
out	d	Output	PIN_M18	5B	B5B_N0	PIN_M18	2.5 V (default)		12mA (default)	1 (default)
out	e	Output	PIN_E16	7A	B7A_N0	PIN_E16	2.5 V (default)		12mA (default)	1 (default)
out	f	Output	PIN_G13	7A	B7A_N0	PIN_G13	2.5 V (default)		12mA (default)	1 (default)
out	q	Output	PIN_G17	7A	B7A_N0	PIN_G17	2.5 V (default)		12mA (default)	1 (default)

## 实验总结

注意判断按键位置时应该加入边缘触发的触发器维持电路稳定